



Aula 07 - Bipolos Não Ôhmicos

Medições Circuito - Figura 18.6

	0	0.5	1	1.5	2	2.5	3	3.5	4	4.5	5	5.5	6
I(mA)	0	0	0	0	0	0.02	0.43	1.9	5.2	11.7	21.7	31.3	40

Medições Circuito - Figura 18.7

	0	1	2	3	4	5	6	7	8	9	10	11	12
I(mA)	0	0	0	0.2	0.8	1.5	2.3	3.2	4	4.9	5.8	6.7	7.6
Vd(V)	0	1	2	2.81	3.19	3.43	3.61	3.75	3.87	3.97	4.06	4.15	4.23
Vr(V)	0	0	0	0.19	0.81	1.57	2.39	3.25	4.13	5.03	5.94	6.85	7.78