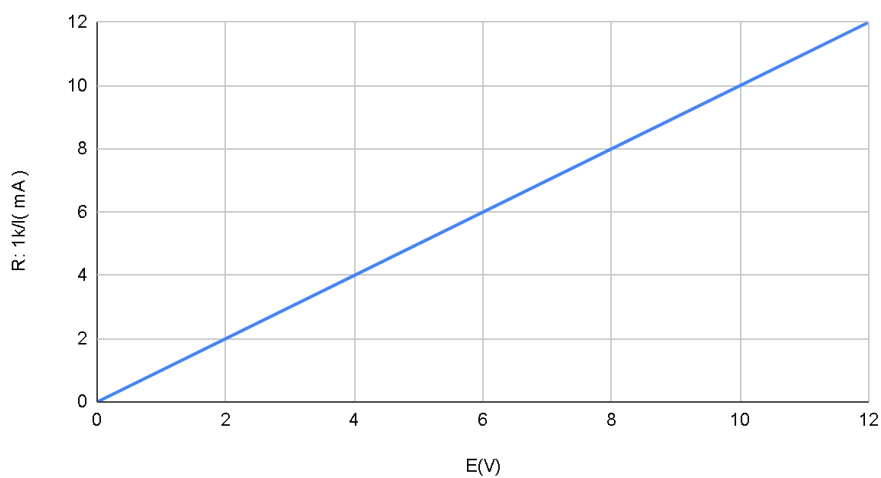


## Aula 06 - Lei de Ohm


### Parte Prática

|      | R: 1k   | R: 2.2k | R: 3.9k | R: 10k  |
|------|---------|---------|---------|---------|
| E(V) | I( mA ) | I( mA ) | I( mA ) | I( mA ) |
| 0    | 0       | 0       | 0       | 0       |
| 2    | 2       | 0,909   | 0,513   | 0,2     |
| 4    | 4       | 1,82    | 1,03    | 0,4     |
| 6    | 6       | 2,73    | 1,54    | 0,6     |
| 8    | 8       | 3,64    | 2,05    | 0,8     |
| 10   | 10      | 4,55    | 2,56    | 1       |
| 12   | 12      | 5,45    | 3,08    | 1,2     |


R: 1k/I( mA ) versus E(V)



E(V) versus R: 2.2k/I( mA )

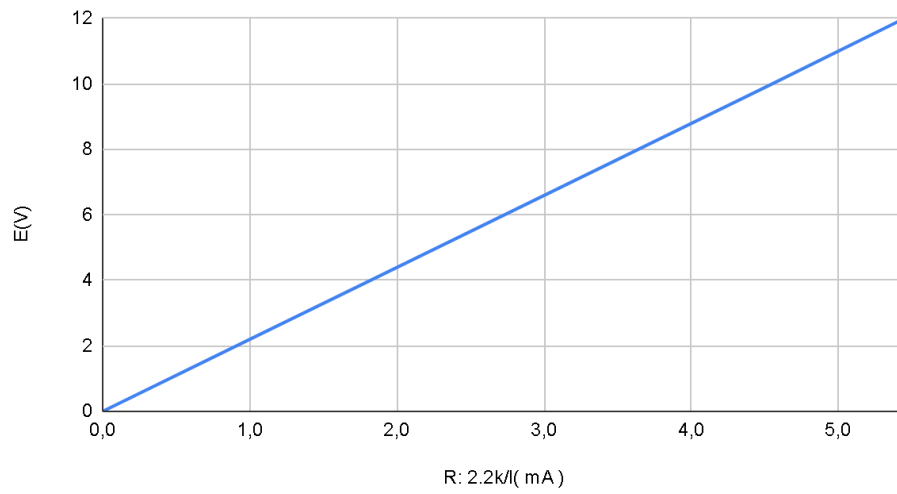

R: 3.9k/I( mA ) versus E(V)

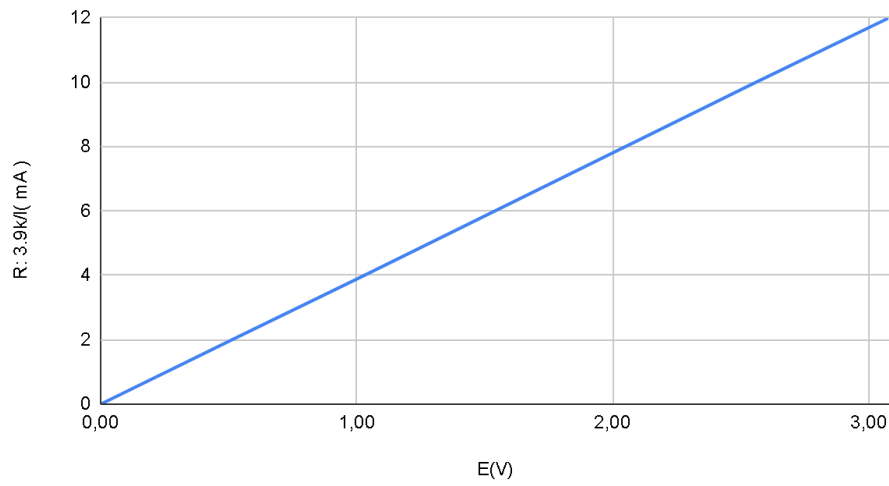

R: 10k/I( mA ) versus E(V)

